

THYRISTORS

→ stay switched on until manually reset

→ symbol: 

→ commonly used for alarms

CAPACITORS

→ stores electricity

→ electrolytic and non-electrolytic



has polarity


→ symbol: 




INTEGRATED CIRCUITS

TIMING CIRCUITS

→ switching actions

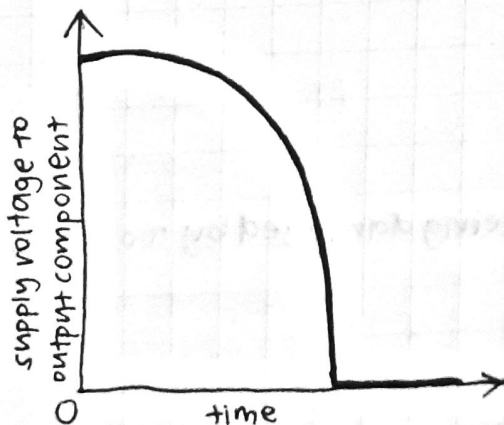

capacitor +
transistor

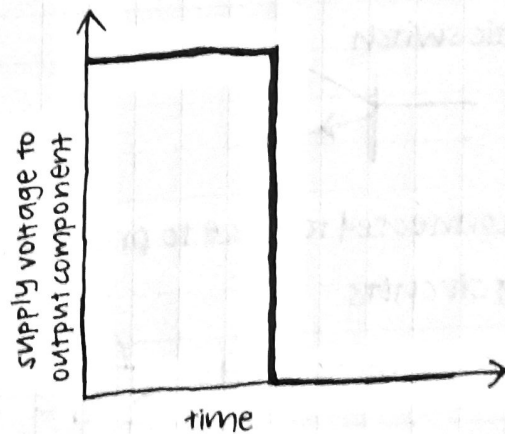

555 timer
+ capacitor

- more accurate
- capable of rapid pulses (e.g. traffic light blinking)